

Name Brian Date \_\_\_\_\_  
Period \_\_\_\_\_ Points available: 

30
----

## Physics

### Worksheet – Ohms Law Problems

$V=IR$     $P=IV$

*\*Most things plugged into a standard wall outlet draw 120V*

1. Which circuit will have brighter bulbs and why? Three identical bulbs connected to a six volt battery in series or 3 identical bulbs connected to a six volt battery in parallel?

Parallel because each circuit branch gets the full 6 volts.

In series, add resistors, current goes down

2. Which battery in question 1 will die out faster and why?

Parallel. - Brighter bulbs = more flow. Battery can only supply a specific amount.

3. What physically happens when a light bulb burns out?

The filament breaks, opening the circuit

4. Which will do more damage; connecting a 110V toaster into a 220V outlet or plugging a 220V toaster into a 110V outlet? Explain your answer.

2 110 into 220 because current will be too high.

In a 220V into a 110, current goes down.

5.	k	V
V = 120V		R
I = 4.2A		

$$V = IR$$

$$120 = 4.2(R)$$

$$R = 28.6 \Omega$$

6.	k	V
P = 1500W		I
V = 120		R

$$P = IV$$

$$1500 = I(120)$$

$$I = 12.5 A$$

$$V = IR$$

$$120 = 12.5 R$$

$$R = 9.6 \Omega$$

7.	k	V
I = 0.25A		V
R = 3800		

$$V = IR$$

$$= .25(3800)$$

$$V = 950 V$$

8.	k	V
I = 7.5A		R
V = 120V		

$$V = IR$$

$$120 = 7.5 R$$

$$R = 16 \Omega$$

9.	k	V
R = 9.6 \Omega		I
V = 240V		

$$V = IR$$

$$240 = I(9.6)$$

$$I = 25 A$$

10.	k	V
V = 12V		R =
I = 0.6A		P =
t = 60s		

$$V = IR$$

$$12 = .6(R)$$

$$R = 20 \Omega$$

$$E = P \cdot t$$

$$= 7.2(60)$$

$$E = 432 J$$

$$P = IV$$

$$= 12(.6)$$

$$P = 7.2 W$$

11.	K	V
	$V = 3.0V$	P
	$I = 320A$	

$$P = IV$$

$$= 3(.320)$$

$$P = 0.96W$$

Oops. Wrong Way!

~~$$P = W$$

$$P = I(IR)$$

$$P = I^2 R$$~~

12.	K	V
	$V = 120V$	
	$P_1 = 850W$	
	$P_2 = 1250W$	

R is higher on low wattage because flow is lower. R is higher

Oops

$$P = IV$$

$$P = IV$$

$$850 = 120(I)$$

$$1250 = 120(I)$$

$$I = 7.1A$$

$$I = 10.4A$$

$$V = IR$$

$$V = IR$$

$$120 = 7.1R$$

$$120 = 10.4R$$

$$R = 16.9\Omega$$

$$R = 11.5\Omega$$

13.	K	V
	$V = 115V$	I
	$P = 110W$	R

$$P = IV$$

$$110 = 115(I)$$

$$I = 0.96A$$

$$V = IR$$

$$115 = 0.96R$$

$$R = 120\Omega$$

14.	K	V
	$V = 120V$	# 100W Bulbs
	$I = 15A$	

$$P = IV$$

$$= 120(15)$$

$$P = 1800W$$

$$P = N(100)$$

$$N = \# \text{ bulbs}$$

$$P = N(100)$$

$$1800 = N(100)$$

$$N = 18 \text{ bulbs}$$